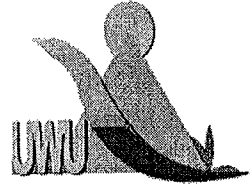


Uva Wellassa University, Sri Lanka
End Semester Examination – September 2011
SCT 363-2 Advanced Electronics



Time: Two (02) hours

Total 04 Questions

Answer All questions.

- 1) a. What are the two main memory types of a microprocessor?
Briefly discuss the function of each category.
- b. Compare and contrast the followings.
- i. SRAM and DRAM.
 - ii. EPROM and EEPROM.
- c. Draw a schematic representation for a single bit memory.
Briefly explain the 'Read' and 'Write' operations using the above representation.
- d. Draw a circuit diagram to show how you would construct a 4kB (2048×16 bit) memory using four 1kB (1024×8 bit) RAM.

(25 Marks)

- 2) a. Define the three types of input/output methods of a microprocessor based system.
- b. What is an "Address Decoder" circuit?
- c. Suppose you are expected to design a microprocessor based system using an 8 bit microprocessor having 16 address lines and other necessary control lines. You are also provided with the following devices together with a switch and a seven segment display to interface with the microprocessor.


Device	Size	Starting Address
EPROM chip	2kB (2048×8 bit)	0000H
RAM chip	4kB (4096×8 bit)	3000H

The switch and the seven segment display should be interfaced using the memory mapped method and their addresses would be 7301H and 7400H respectively.

- i. Draw the memory map of the system.
- ii. Draw a circuit diagram of the system showing all the address decoding circuits. (You may use additional gates if necessary)

(25 Marks)

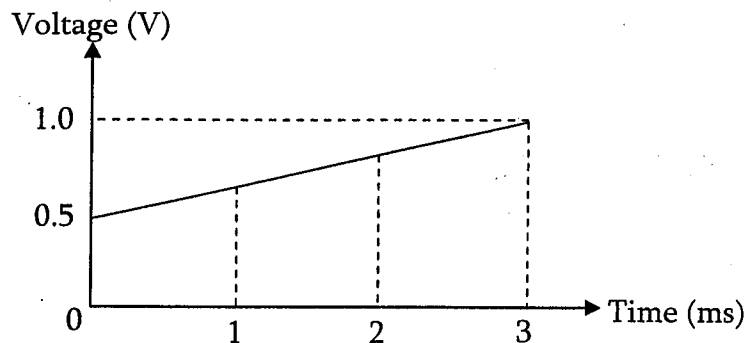
- 3) a. Briefly explain how information is lost during the process of analog to digital conversion (ADC). What is the importance of the sampling theorem in this respect?
- b. Describe the principle of operation of a dual slope ADC. How does it avoid the problems associated with single slope ADC?
- c. An 8-bit dual slope ADC with 0.1 ms charging time is used to digitize the signal shown below. Calculate the conversion time in each case if the ADC is started at $t = 0, 1$ and 2 ms .



- d. Discuss the nature of the error introduced into the measurements due to the variation of the input signal during the charging period. Suggest a method to solve this problem (without changing the ADC speed).

(25 Marks)

- 4) a. What is a first order active filter?
- b. Plot a graph of gain, $\{|e_o / e_i|\}$, against frequency for a simple first order passive low-pass CR filter and use this graph to show that,
- at f_c the gain is 3 dB less than its DC value.
 - at frequencies higher than $2f_c$ the output declines at 20 dB/decade .
- c. Using response curves, relevant equations and circuit model explain
- first order band-pass passive CR filter circuit.
 - first order high pass OPAMP filter circuit.
- d. For the following OPAMP circuit, find the expression for V_o .

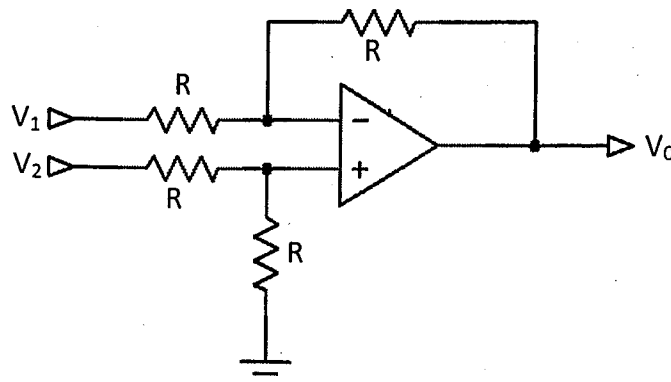

(25 Marks)