

Time: Two (02) hour

Total 04 questions

Answer all questions

Do not remove this paper from the examination hall

1.

- a) Briefly explain the difference between an active filter and a passive filter.
- b) Identify the circuit diagram in figure 01.

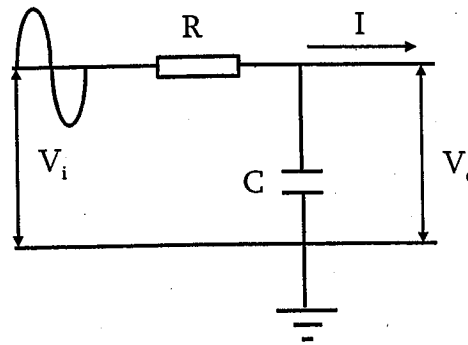


Fig. 01

- c) Plot the graph of gain (V_o/V_i), against frequency for above circuit.
- d) Using response curves, relevant equations and circuit model explain
 - i. First order band-pass passive CR filter circuit.
 - ii. First order low pass OPAMP circuit.
- e) For the following OPAMP circuit find the expression for V_o .

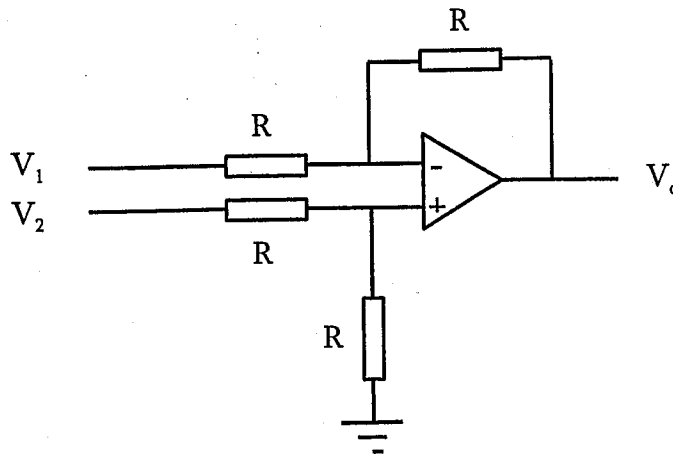


Fig. 02

(25 marks)

2.

- a) State the sampling theorem in signal transmission.
- b) Briefly explain how information is lost during the process of analog conversion (ADC).
- c) Compare the single slope ADC with dual slope ADC.
- d) Draw the typical schematic diagram of a single slope ADC.

(25 marks)

3.

- a) Draw a schematic representation for a single bit memory. Briefly explains the "Read" and "Write" operations using the above representation.
- b) Write short notes for three (03) of the following topics
 - i. SRAM
 - ii. DRAM
 - iii. EPROM
 - iv. EEPROM
- c) Draw the circuit diagram to show how you would construct a 2kB (2048*8 bit) memory using two 1kB (1024*8 bit) RAM.

(25 marks)

4.

- a) Briefly explain the two types of address decoding methods.
- b) What is parity checking in memory address decoding?
- c) Suppose you are expected to design a microprocessor based system using an 8 bit microprocessor having 16 address lines and other necessary control lines. You are also provided with the following devices together with a switch to interface with the microprocessor.

Device	Size	Starting address
Flash memory	2kB (2048*8 bit)	0000H
EEPROM chip	2kB (2048*8 bit)	2000H

The switch should be interfaced using the memory mapped method. Its address is 7301H.

- i. Draw the memory map of the system
- ii. Draw a circuit diagram of the system showing all the address decoding circuits. (You may use additional gates if necessary)

(25 marks)