

**Uva Wellassa University of Sri Lanka**  
**Faculty of Science and Technology**  
**Department of Computer Science and Technology**  
**200 level 2<sup>nd</sup> Semester Examination – Dec./Jan. 2016/17**  
**CST231-2 Microelectronics**



**Instructions to candidates**

**Duration:** Two (02) hours

**Number of questions:** Four (04)

**Mark allocation:** 100

**Answer all questions**

- 1.
- a. Discuss the advantages of Digital signals compared to Analog signals. (3 mark)
  - b. Explain the following terms with respect to signal processing using appropriate examples.
    - i. Maximum frequency
    - ii. Quantization error (6 mark)
  - c.
    - i. Briefly explain the process of analog to digital conversion using appropriate hypothetical values. (3 mark)
    - ii. Assume the bit-rate of a compressed audio file is specified as 92 Kbps while the compression ratio is approximately 9:1. Provided that the sampling rate is 44.1 Khz. Determine the bit-depth (resolution) of the particular audio. (5 mark)
  - d.
    - i. Differentiate between Low-Pass frequency filters and High-Pass frequency filters. (4 mark)
    - ii. Explain the functionality of above d.(i) listed frequency filters using circuit diagrams and frequency response curves. (4 mark)
- 2.
- a. Briefly explain how to produce different types of (P and N type) semiconductors using intrinsic semiconductor materials. (4 mark)
  - b. Explain the phenomenon of 'diffusion' which occurs in formation of a potential barrier at any P-N junction. (4 mark)
  - c.
    - i. List five (05) Three-terminal semiconductor components. (5 mark)
    - ii. Explain the improved characteristics of any two (02) components selected from the list produced in above c.(i) using circuit diagrams or characteristic curves. (4 mark)
  - d. The forward-bias  $i-v$  relationship of a typical P-N junction is given below:

$$i = I_s (e^{v/V_T} - 1) \text{ while } V_T = kT/q$$



- i. Define the terms of the formulae. (3 mark)
- ii. A silicon diode is said to be a 1 mA components exhibits a forward voltage of 0.67 V. Given that the values of  $k$ ,  $V_T$  and  $q$  are  $8.62 \times 10^{-5}$  eV/K , 25.3 mV (at room temperature) and  $1.60 \times 10^{-19}$  coulomb, respectively. Evaluate the junction scaling constant (saturation current). (5 mark)

3.

- a. State the conditions to be satisfied in order to switch in between the Cut-off Region (where the transistor acts as an off switch) and the Active Linear Region (where the transistor acts as a current amplifier) of a typical NPN type Bipolar Junction Transistor.

Use the terms  $V_{BE}$  (Base-Emmitter Voltage),  $V_{FB}$  (Forward Bias Voltage),  $I_B$  (Base current) and the derived relationship between  $I_B$ ,  $I_{C,max}$  (The maximum current that will flow across collector) and  $\beta$  (Common Emitter current gain) for each status. (8 mark)

b.

- i. A bipolar NPN transistor has a DC current gain ( $\beta$ ) value of 50. Calculate the base current  $I_B$  required to switch a resistive load of 9 mA. (2 mark)
- ii. A NPN transistor has a DC base bias voltage,  $V_B$  of 10 V and an input base resistor,  $R_B$  of 150 K $\Omega$ . What would be the value of the base current ( $I_B$ ) into the transistor? Clearly state any assumptions you made. (3 mark)

- c. Consider the following circuit diagram (Figure 01).

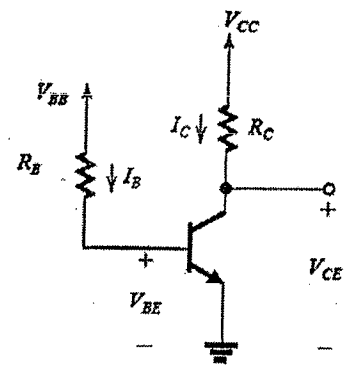


Figure 01: A transistor circuit

Assume that at the edge of saturation  $V_{CE} = 0.6$  V,  $V_{BE}$  remains constant at 0.7 V. The transistor DC current gain  $\beta$  is specified to be 100.

For the circuit shown in Figure 01, determine the value of the voltage  $V_{BB}$  that results in the transistor operating at the edge of saturation. Given that  $V_{CC} = 10$  V,  $R_B = 12$  K $\Omega$ ,  $R_C = 2.5$  K $\Omega$ .

(4 mark)

- d. Consider the following schematic diagram of the amplifier circuit (Figure 02).

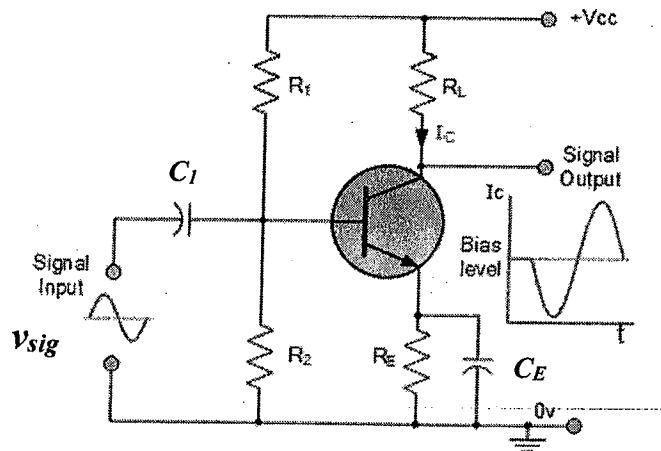


Figure 02: A transistor amplifier circuit

- i. Identify the class and the configuration of the amplifier in Figure 02. (2 mark)
  - ii. What is the functionality of capacitor  $C_1$ ? (3 mark)
  - iii. What is the functionality of capacitor  $C_E$ ? (3 mark)
- 4.
- a. Compare and contrast Field-Effect Transistors (FETs) against Bipolar Junction Transistors (BJTs). (3 mark)
  - b. List two (02) applications from each: Junction Field-Effect Transistors (JFETs) and Metal-Oxide-Semiconductor FETs (MOSFETs). (4 mark)
  - c. The Drain current  $I_D$  of a N-Type JFET for any given bias point in the saturation or active region can be calculated using
 
$$I_D = I_{DSS} [ 1 - (V_{GS} / V_{GS(\text{cut-off})}) ]^2$$
    - i. Define the terms of the formula. (3 mark)
    - ii. If a JFET has a Drain current of 6 mA when  $I_{DSS} = 4$  mA and  $V_{GS(\text{cut-off})} = -5.5$  V, find the value of  $V_{GS}$ . (4 mark)
  - d.
    - i. What are the two (02) basic configurations of operational amplifiers? (4 mark)
    - ii. Using appropriate circuit diagrams, explain how to construct a comparator using an operational amplifier. (5 mark)
    - iii. List three (02) applications of operational amplifiers except voltage comparators. (2 mark)