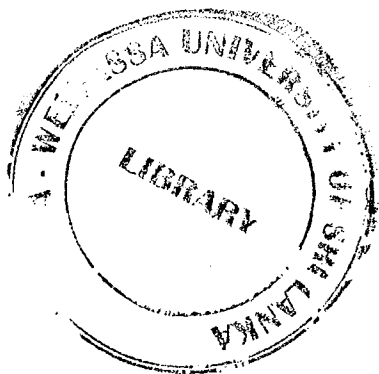




Uva Wellassa University, Sri Lanka
End Semester Examination – March 2011
SCT 361-2 Digital and Analog Electronics



Time: Two (02) hours

Total 06 Questions

Answer 02 questions from Part-A and 02 from Part-B

PART - A

- 1) a. What are product terms and sum terms of combinational circuit?
- b. i. Convert $Y = ABCD + A'BC + B'C'$ into a sum of minterms by algebraic method.
ii. Convert $Y = AB + B'CD$ into a product of maxterms by algebraic method.
- c. Design a logic circuit with four inputs A, B, C and D where the output is to be high only when majority of the inputs are high. Draw the final circuit using only NOR gates.
- d. By using Karnaugh map simplification, derive the logic equations for a circuit that will add two 2-bit binary numbers, $(A_1 A_0)_2 + (B_1 B_0)_2$, and produce the sum bits $(S_1 S_0)_2$ and the carry output bit C_1 , as shown below.

$$\begin{array}{r} A_1 A_0 \\ + B_1 B_0 \\ \hline C_1 S_1 S_0 \end{array}$$

(25 marks)

- 2) a. What is a multiplexer? Draw the circuit diagram, truth table and give the Boolean equation describing the output, of a 4-to-1 multiplexer.
- b. What is the difference between a decoder and a demultiplexer?
- c. What is a full-adder? Implement a full-adder circuit using NOR gates only.
- d. Use two-input XOR gates to produce the parity generation and checking system that ensures the 4-bit data sent over a serial link is transmitted and received as an odd parity word.
- e. An 8-to-1 MUX has inputs A, B and C connected to selection lines S_2, S_1 and S_0 respectively. The data inputs I_0 to I_7 are connected as,
 $I_1 = I_2 = I_7 = 0, I_3 = I_5 = 1, I_0 = I_4 = D$ and $I_6 = \bar{D}$
Determine the Boolean expression of the MUX output.

(25 marks)

- 3) a. What is the difference between a latch and a flip-flop?
- b. Determine how the circuit shown in Fig. 1 functions as a JK-type flip-flop. Under what input conditions a problem may occur?

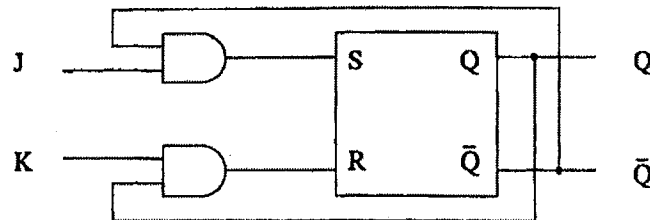


Fig. 1

- c. Fig. 2 shows a master-slave flip-flop in which the C input is a square-wave clock signal. Analyze its operation.


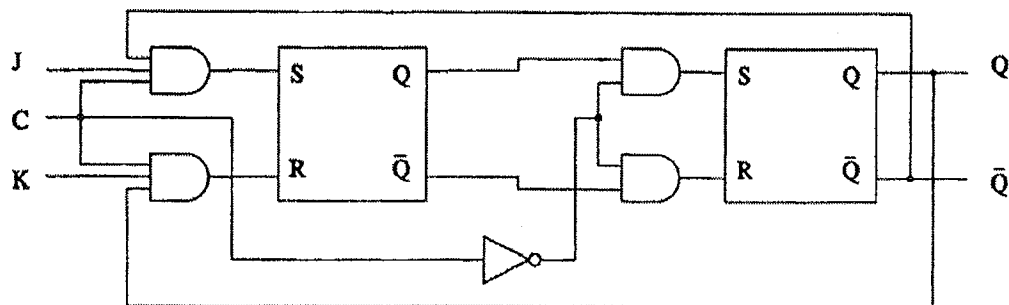


Fig. 2

- d. Explain the operation of 4-bit bidirectional shift register with the help of a neat diagram.
- e. Design a 4-bit binary ripple counter using negative edge-triggered J-K flip-flops and draw the timing diagram.

(25 marks)

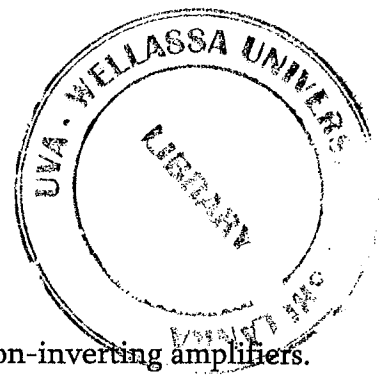

PART - B

- 4) a. Explain how an OPAMP can be used as a comparator.
- b. Draw basic schematic diagrams of both inverting and non-inverting amplifiers.
- c. Derive expressions for closed loop gain (G) of both inverting and non-inverting amplifiers.
- d. Identify the circuit given in Fig. 3. Derive an equation for its output in terms of inputs and component values. Describe functionality and practical applications.

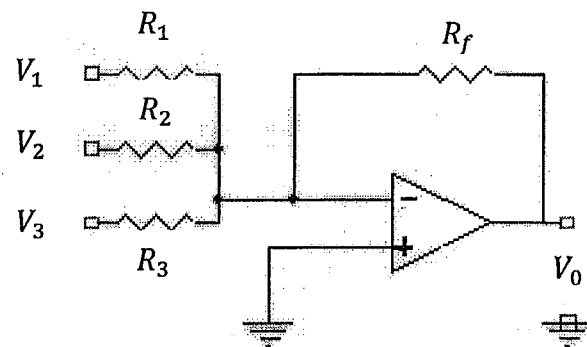


Fig.3

- e. Explain the basic integrator circuit using ideal OPAMPs.

(25 marks)

- 5) a. By using two diodes and relevant components draw voltage doubler circuit. Explain its function.
- b. The $6.8V$ Zener diode in the circuit of Fig.4 is specified to have $V_Z = 6.8V$ at $I_Z = 5mA$. The Zener diode can be replaced with its equivalent circuit model shown in Fig.5, where $r_z = 20\Omega$. The supply voltage V^+ is nominally $10V$ but can vary by $\pm 1V$.

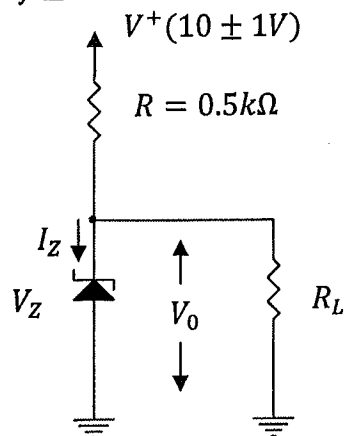


Fig.4

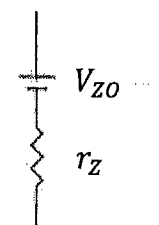


Fig.5

- i. Find V_{Z0} of equivalent circuit model.
- ii. Find V_0 with no load and with V^+ at its nominal value.
- iii. Find the change in V_0 resulting from the $\pm 1V$ change in V^+ .
- iv. Find the change in V_0 resulting from connecting a load resistance R_L that draws a current $I_L = 1mA$.
- v. Find the change in V_0 when $R_L = 2k\Omega$.
- vi. Find the change in V_0 when $R_L = 0.5k\Omega$.
- vii. What is the minimum value of R_L for which the diode still operates in the breakdown region? Where knee current, $I_{ZK} = 0.2mA$.

(25 marks)

- 6) a. What is a Darlington pair? Draw a Darlington pair circuit and derive an expression for current gain (β).
- b. Obtain expressions for I_{C2} and I_{B1} for the circuit in Fig.6. Discuss the applications of it.

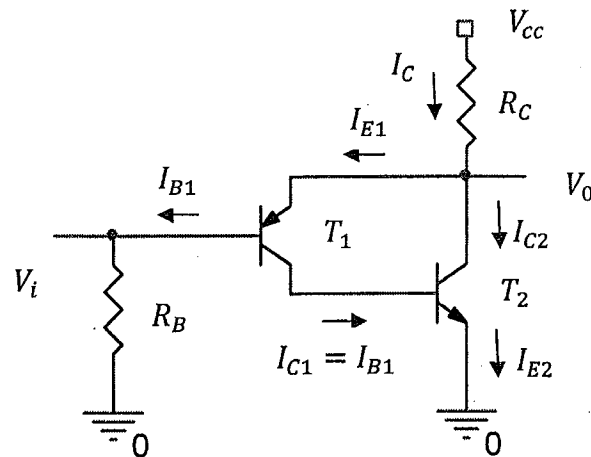


Fig.6

- c. Using relevant circuit diagram and characteristic curves explain the BJT's function as a switch.

(25 marks)