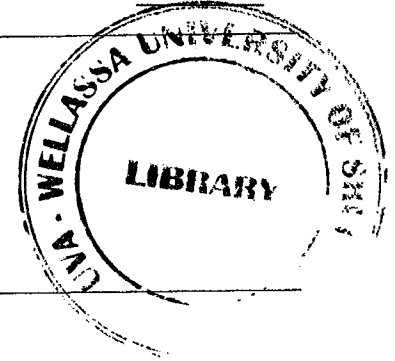


Uva Wellassa University of Sri Lanka
Faculty of Science and Technology
Department of Computer Science and Technology
200 Level 2nd Semester Examination – Jan. / Feb. 2016
CST 231-2 Microelectronics



Instructions to candidates:

Duration: Two (02) hours

Number of questions: Four (04)

Answer all questions

Mark allocation: 100

Calculators are **allowed**.

1.
 - a. Discuss the necessity of converting Analog signals in to Digital. (3 mark)
 - b. Explain the meaning of the following terms with respect to signal processing using appropriate examples:
 - i. Sampling rate
 - ii. Bandwidth
 - iii. Bit depth (6 mark)
 - c.
 - i. Using an appropriate example, discuss the impact of sampling rate for the quality of the output of a typical analog to digital conversion. (3 mark)
 - ii. The bit-rate of a compressed audio file is specified as 128 kbps while the compression ratio is approximately 10:1. Provided the fact that the sampling rate is 44.1 Khz. Determine the bit-depth (resolution) of the particular audio. (5 mark)
 - d.
 - i. What are the **four (04)** major types of frequency filters? (4 mark)
 - ii. Explain the functionality of above (i.) listed frequency filters using frequency response curves. (4 mark)
2.
 - a. Briefly explain the process of **doping** in order to manufacture P and N type semiconductors from intrinsic semiconductor materials. (4 mark)
 - b. Explain the phenomenon of **diffusion** occurs at any P-N junction prior to formation of the depletion layer. (4 mark)
 - c.
 - i. List **five (05)** Two-terminal semiconductor devices. (5 mark)
 - ii. Explain the improved characteristics of any **two (02)** devices selected from the list produced in above (i.) using characteristic curves. (4 mark)

d. The forward-bias $i-v$ relationship of a typical P-N junction is given below:

$$i = I_s (e^{V/V_T} - 1) \text{ while } V_T = kT/q$$

i. Define the terms of the formulae.

(3 mark)

ii. A silicon diode said to be a 1 mA device exhibits a forward voltage of 0.7 V. Given that the values of k , V_T and q are 8.62×10^{-5} eV/K, 25.3 mV (at room temperature) and 1.60×10^{-19} coulomb, respectively. Evaluate the junction scaling constant (saturation current).

(5 mark)

3.

a. State the conditions should satisfy to switch between the following status of a NPN type Bipolar Junction Transistor.

Hint: Use the terms V_{BE} (Base-Emmitor Voltage), V_{FB} (Forward Bias Voltage), I_B (Base current) and the relationship between I_B , $I_{C,max}$ (The maximum current that will flow across collector) and β (Common Emitter current gain) at each status.

- i. Cut-off Region: Transistor acts as an off switch
- ii. Active Linear Region: Transistor acts as a current amplifier
- iii. Saturation Region: Transistor acts as an on switch
- iv. Q-Point (on DC Load-Line)

(8 mark)

b.

i. A bipolar **NPN** transistor has a DC current gain (β) value of 200. Calculate the base current I_B required to switch a resistive load of 6 mA.

(2 mark)

ii. A NPN Transistor has a DC base bias voltage, V_B of 11V and an input base resistor, R_B of 100k Ω . What would be the value of the base current (I_B) into the transistor? Clearly state any assumptions you made.

(3 mark)

c. Consider the following circuit diagram (Figure 01).

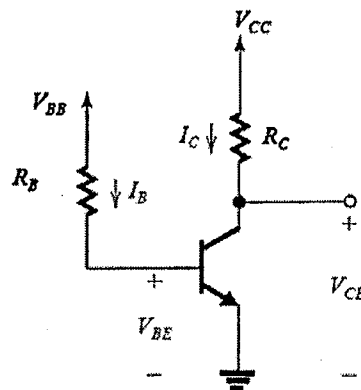


Figure 01: A transistor circuit

For the circuit shown in Figure 01, determine the value of the voltage V_{BB} that results in the transistor operating in following status. Given that $V_{cc} = 12$ V, $R_B = 15$ k Ω , $R_C = 1.5$ k Ω .

(Assume that at the edge of saturation $V_{CE} = 0.3 \text{ V}$, V_{BE} remains constant at 0.7 V . The transistor DC current gain β is specified to be 50.)

- i. At the active mode with $V_{CE} = 5 \text{ V}$
- ii. At the edge of saturation

(4 mark)

d. Consider the following schematic diagram of the amplifier circuit (Figure 02).

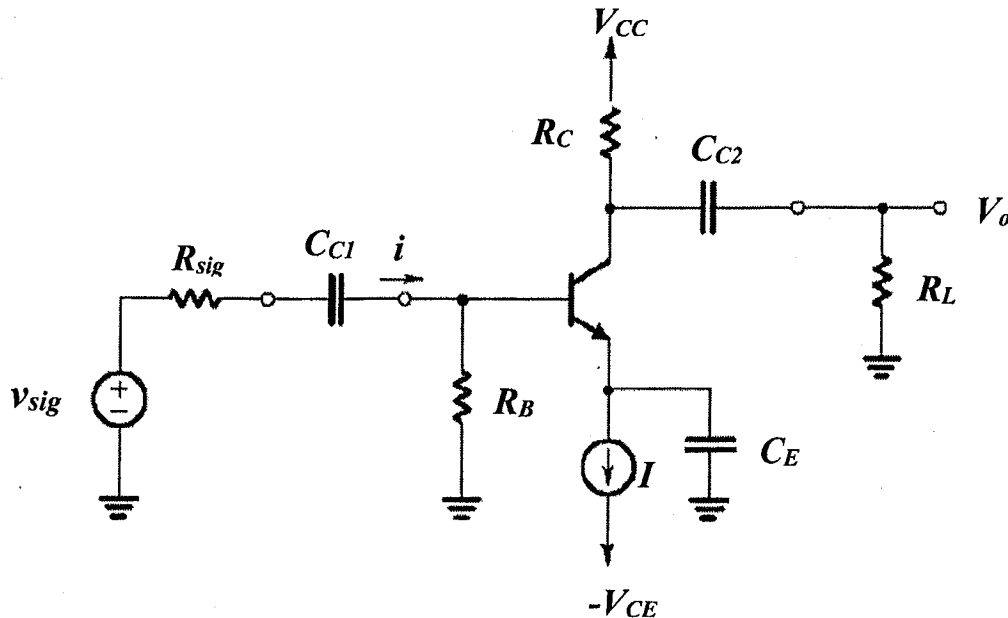


Figure 02: A transistor amplifier circuit

- i. Identify the class and the configuration of the amplifier in Figure 02. (2 mark)
- ii. What is the functionality of capacitors C_{C1} and C_{C2} ? (3 mark)
- iii. What is the functionality of capacitors C_E ? (3 mark)

4.

- a. What are the key advantages of FETs (Field-Effect Transistors) compared to BJT (Bipolar Junction Transistors)? (3 mark)
- b. Compare and contrast JFET (Junction Field-Effect Transistor) against MOSFET (Metal-Oxide-Semiconductor FET). (4 mark)

c. The Drain current I_D of a N-Type JFET for any given bias point in the saturation or active region can be calculated using

$$I_D = I_{DSS} [1 - (V_{GS} / V_{GS(cut-off)})]^2$$

- i. Define the terms of the formula. (3 mark)
- ii. If a JFET has a drain current of 9 mA when $I_{DSS} = 3 \text{ mA}$ and $V_{GS(cut-off)} = -6 \text{ V}$, find the value of V_{GS} . (4 mark)



- d.
- i. Define the parameters associated with an operational amplifier and specify their ideal values. (4 mark)
 - ii. Using appropriate circuit diagrams, explain how to construct an op-amp comparator to compare an analog voltage V with a fixed reference value V_{REF} . (4 mark)
 - iii. Explain what is meant by **Hysteresis** using an appropriate example. (3 mark)