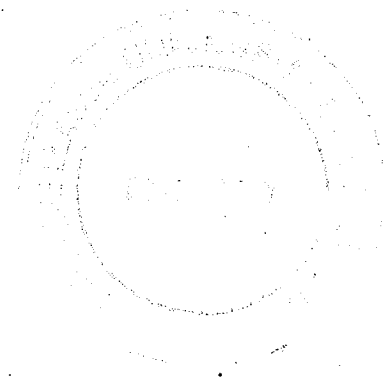




Uva Wellssa University, Sri Lanka  
Btech. Degree Programme  
End Semester Examination- Semester 1  
December -2008  
ENG 302-2 – Principles of Electricity



Answer four (4) questions only

Time: Two (02) hours

**Question1.**


- 1) Explain active circuit elements and passive circuit elements. Give two examples for each?
- 2) What are the advantages of sinusoidal varying voltages?
- 3) A 5 pF capacitor is connected series with a coil having internal resistance of 50  $\Omega$  and 150  $\mu\text{H}$  inductance across an alternating voltage of  $V = 212.1 \sin(\pi 10^6 t + \pi/4)$  Volts. Calculate
  - a) RMS value of the supplied voltage in polar coordinates,
  - b) The circuit impedance,
  - c) RMS value of the current flowing in polar coordinate,
  - d) The Circuit phase angle,
  - e) Voltage across the resistor,
  - f) Voltage across the inductor,
  - g) Draw the phase diagram for the circuit,

**Question2.**

- 1) What is a bilateral network?
- 2) State Thevinin's theorem and Nortan's theorem?
- 3) For the network shown in figure, derive
  - a) The Thevinin's equivalent circuit.
  - b) The Nortan's equivalent circuit.

If a 6  $\Omega$  resistance is connected across A and B. Determine the current flowing in 6  $\Omega$  resistance

- c) Using Thevinin's theorem.
- d) Using Nortan's theorem.

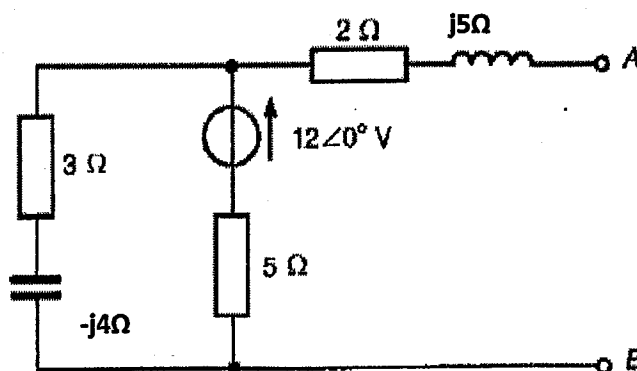

**Question3.**


- 1) What are the advantages of transmitting power in three phases?
- 2) What is a balance three phase system? What can you say about the line current and line voltage in each phase in a balance three phase system?
- 3) A three phase star connected alternator supplies a delta connected load, each phase of which has a resistance of  $30\ \Omega$  and inductive reactance  $40\ \Omega$ . If the line voltage is  $400\text{V}$  then
  - a) Convert the delta connected load to a star connected load and draw the single circuit of the three phase system.

Using the single circuit of the three phase system calculate

- b) The line current supplied by the alternator.
- c) Active power and the KVA of the alternator, neglecting losses in the line between the alternator and load.

**Question4.**

- 1) Explain what is meant by transient condition of an electric circuit?
- 2) What are the advantages of using Laplace transform for analyzing transient conditions of an electric circuit?
- 3) For the circuit shown in the following figure obtain an equation which shows how current varies with time using Laplace Transform. Assume zero initial conditions when the switch is closed.

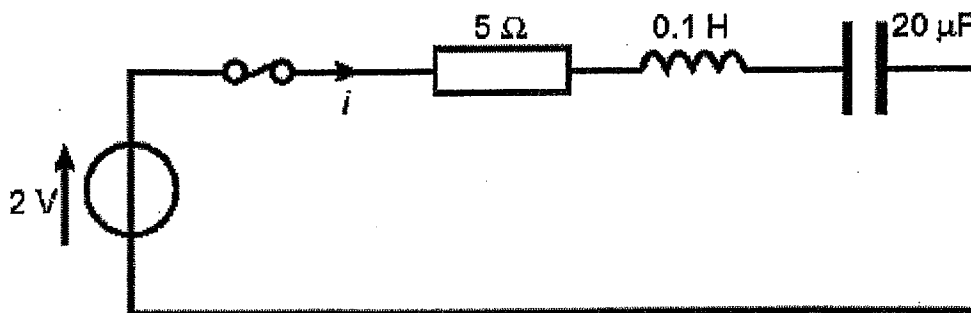

**Question5.**

- 1) Explain resonance in an electric circuit?
- 2) What are the three main method of defining resonance condition in an electric circuit?  
Explain behavior of impedance, current and voltage for each case.
- 3) Find the followings for the circuit in the figure
  - a)Unity power factor resonance frequency?
  - b) Resonance frequency when the circuit impedance becomes maximum?

$R= 20 \Omega$  ,  $L =10 \text{ mH}$  ,  $C= 4\mu\text{F}$

