

Time: One (01) hour

Total 04 Questions.

Answer All questions.

- 1) a. Define the following terms with reference to sinusoidal alternating current.
- Average value
 - rms value
- b. Determine the Average value, rms value for the wave form given in Fig Q1.


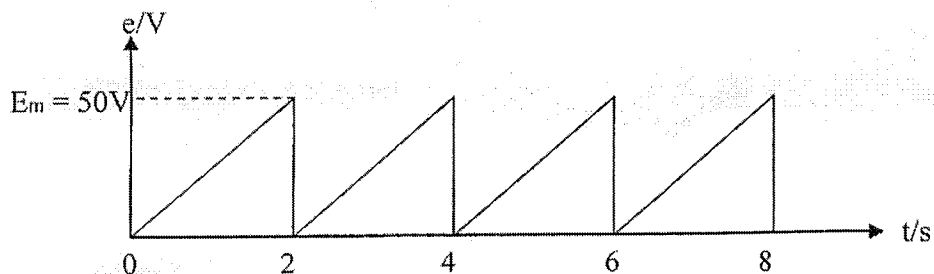


Fig Q1

(25 Marks)

- 2) a. Obtain an expression for resonant frequency (f_0) of a series L - C circuit.

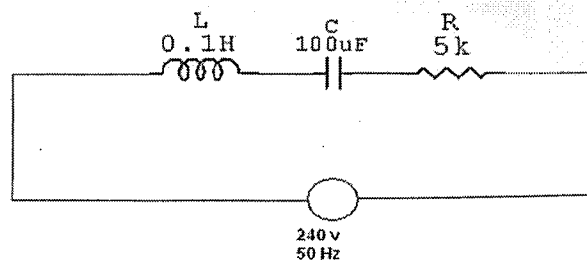

FigQ2

- b. A series resonant circuit has a 0.1 H inductance, a 100 μ F capacitor and a 5 k Ω resistor connected across a 240 V, 50 Hz supply line. Calculate,
- inductive reactance
 - capacitive reactance
 - total impedance
 - current
 - voltage across each part of the circuit
 - true power and power factor

(25 Marks)

3) A coil is wound uniformly with 200 turns over a steel ring of relative permeability 900 having a mean circumference length of 50 cm and a cross sectional area of 5 cm² (Fig Q3). If the coil has a resistance of 125Ω and is connected to 250 V DC supply, calculate

- Current through the coil
- The coil m.m.f.
- The coil magnetic field strength
- Total magnetic flux
- Reluctance of the ring

Where permeability of free space is $(\mu_0) = 4\pi \times 10^{-7} \text{ H/m}$


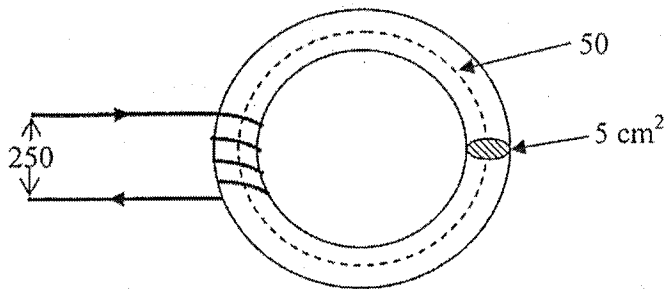


Fig Q3

(25 Marks)

4) a. Briefly explain the losses of the transformer

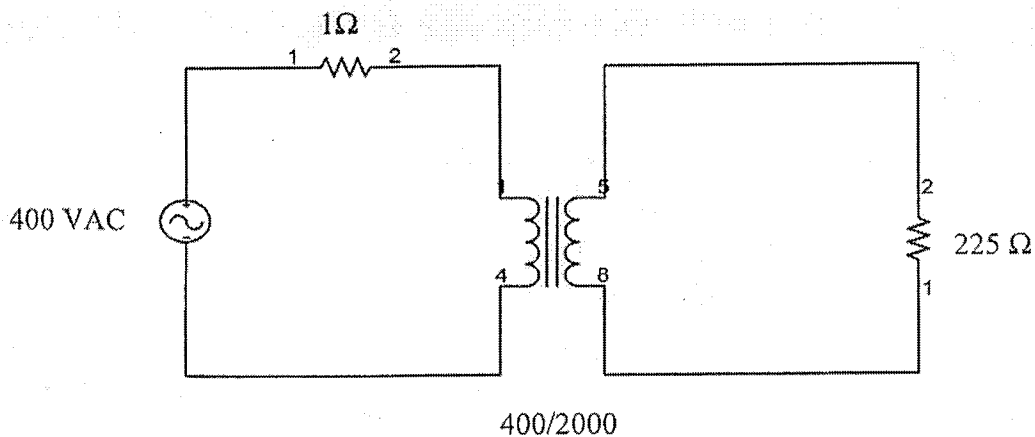b. A single phase 400/2000 transformer has a resistance of 1Ω connected in series with primary winding and a 225 Ω resistor connected across its secondary winding. Calculate the current in the secondary side when the circuit is supplied at 400 VAC.



(25 Marks)