

Uva Wellassa University of Sri Lanka
Faculty of Science and Technology
Department of Computer Science and Technology
End Semester Examination – August/September 2014



CST 231 – 2 Microelectronics

Number of questions: Four (04)
 Answer all questions
 Time allocation: Two (02) hours
 Total mark: 100

1.
 - a. What is the purpose of a transducer? (3 mark)
 - b. A signal source has an open-circuit voltage of **10mV** and a short-circuit current of **10μA**. What is the source resistance? (3 mark)
 - c. What is a digital signal? (3 mark)
 - d. Consider a **4 bit** digital word **b₃b₂b₁b₀** in a format called unsigned-magnitude and it does not represent any negative values. This digital word represents an analog signal (v_A) which varies between 0V and 15V.
 - i. Give digital word corresponding to $v_A=0V, 1V, 2V$ and 15V. (4 mark)
 - ii. What does happen to v_A if the value of b_0, b_1, b_2 and b_3 is changed from 0 to 1? (1.5x4=6 mark)
 - e. If $v_A=5.2V$, what is the digital code expected? What is an error percentage? (6 mark)

2.

- a. Construct three input AND gate and OR gate using diodes (You can use your own notations for inputs and output).
(2x3=6 mark)

- b. In the ideal-diode circuit shown in the Figure 1, v_i is **1KHz, 10V** peak sine wave. Sketch the resultant waveform at v_o . What are its positive and negative peak values?
(5 mark)

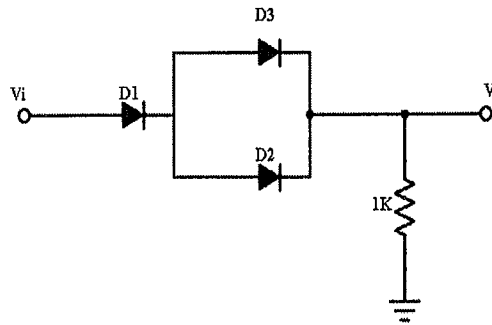



Figure 1. Ideal-diode circuit

- c. List and explain all steps in IC fabrication. (14 mark)


3.

- a. Draw the simplified structure of **npn** bipolar junction transistor (indicate all junctions). Write all the modes of bipolar junction transistors and corresponding bias condition of each **pn** junctions. (9 mark)

- b. Find the values for the labeled nodes voltage and branch current for Circuit 2 and Circuit 3. Write all necessary steps.
 (Assume $\beta = 100$ and $|V_{BE}| = 0.7V$.) (8 x 2 = 16 mark)

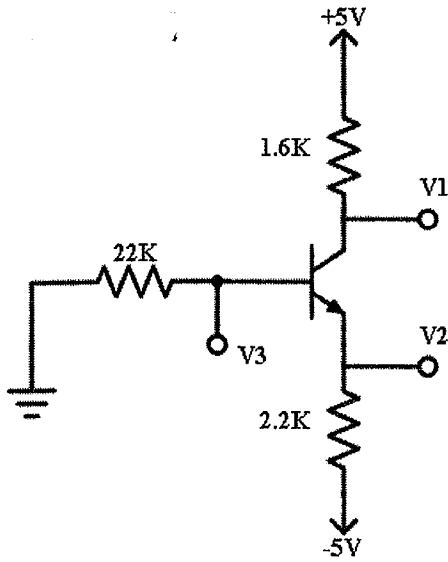

Circuit 1

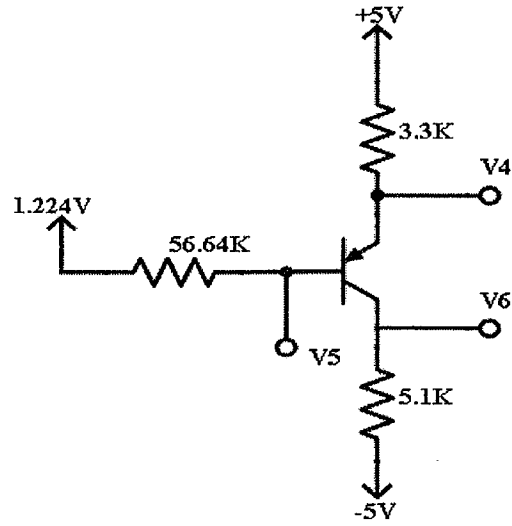

Circuit 1

4.

- Construct CMOS logic circuits for two inputs NOR gate and two inputs NAND gate. (8 mark)
- Sketch a CMOS logic circuit that realizes the function $y = \overline{A(B + CD)}$. (8 mark)
- Draw the graph of the voltage transfer characteristic of an inverter. (5 mark)
- Draw the circuit diagram of the CMOS digital logic inverter. (4 mark)