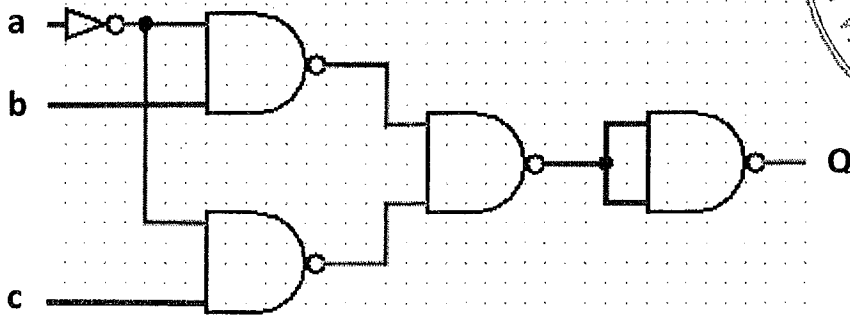


1.
  - a. Define the terms **Boolean expression** and **truth table**. (4 mark)
  - b. What are the advantages of Boolean expression simplification? (3 mark)
  - c. Consider the logic circuit below to answer the following questions.



- i. Derive the Boolean expression and draw up the truth table for the circuit above. (4.5 mark)
- ii. Simplify the Boolean expression derived in part c. i. to its simplest form using any applicable Boolean laws and theorems. (4.5 mark)
- iii. Draw the circuit diagram for the simplified Boolean expression. (3 mark)
- iv. Simplify the Boolean expression derived in part c. i. to its simplest form using K-map. (3.5 mark)
- v. Draw up the truth table for simplified circuit and prove that the two (02) circuits are equivalent. (4 mark)

2.
  - a.
    - i. Define the term **circuit** and list the components of a circuit. (5 mark)
    - ii. Design a 4-bit parallel Adder and briefly describe how two (02) binary numbers 1001<sub>2</sub> and 0101<sub>2</sub> can be added to produce the output using a graphical explanation. (6 mark)
  - b.
    - i. Mention the two (02) types of sequential circuits and differentiate them. (5 mark)
    - ii. What is the drawback of S-R flip flop and how it is overcome by D flip flop? (4 mark)
    - iii. Briefly describe the memory states of S-R flip flop by providing suitable examples. (7 mark)

3.

- a. What is a microprocessor? List the three (03) types of information it can carry. (5 mark)
- b. List six (06) types of instructions which can be supported by 8086 architecture? (5 mark)
- c. Briefly describe the pipelining technique in 8086 architecture. (6 mark)
- d. Find out the physical address of a data stored in **Data** memory where DS = 1200, IP = 124 and SI = 240. (3 mark)
- e. i. Explain the process takes place after executing the following instruction. Assume that BL = 05<sub>H</sub> and CL = 10<sub>H</sub>. (4 mark)

**ADD BL, CL;**

- ii. Rewrite the above instruction to do the same function using only one (01) register. (3.5 mark)

