

Uva Wellassa University, Sri Lanka
Faculty of Science and Technology
Science and Technology Degree Program
2nd Semester Examination – September / October 2013



SCT 369-2 Electric Power and Machines

Number of questions: three (03)

Answer all questions

Time allocation: Two (02) hour

Total marks allocated: 100

All symbols used have their standard definitions

1.

- a. Explain how a shunt DC motor responds to an increasing external load.
(03 marks)
- b. A 50 hp, 250 V, 1200 rad/min DC shunt motor with compensating windings has an armature resistance (including brushes, compensating windings and interpoles) of 0.06Ω . Its field circuit has a total resistance $R_{adj} + R_f$ of 50Ω , which produces no-load speed of 1200 rad/min. There are 1200 turns per pole on the shunt field winding. Determine the speed of this motor when its input current is,
- i. 100 A.
 - ii. 200 A.
 - iii. 300 A.
- (12 marks)
- c. A separately-excited generator develops a no-load e.m.f. of 150 V at an armature speed of 20 rev/sec and a flux per pole of 0.10 Wb. Determine the generated e.m.f. when,
- i. the speed increases to 25 rev/sec and pole flux remains unchanged
 - ii. the speed remains at 20 rev/sec and the pole flux is decreased to 0.08 Wb
 - iii. the speed increase to 24 rev/sec and the pole flux decreased to 0.07 Wb
- (15 marks)

2.

- a. The secondary winding of a transformer shown in Figure 1 has a terminal voltage of $V_s(t) = 282.8 \sin 377t$ V. The turns ratio is 100:200. The secondary current of the transformer is, $i_s(t) = 7.07 \sin(377t - 36.87^\circ)$ A. The impedances of this transformer referred to the primary side are

$$R_{eq} = 0.20 \Omega$$

$$R_c = 300 \Omega$$

$$X_{eq} = 0.750 \Omega$$

$$X_M = 80 \Omega$$

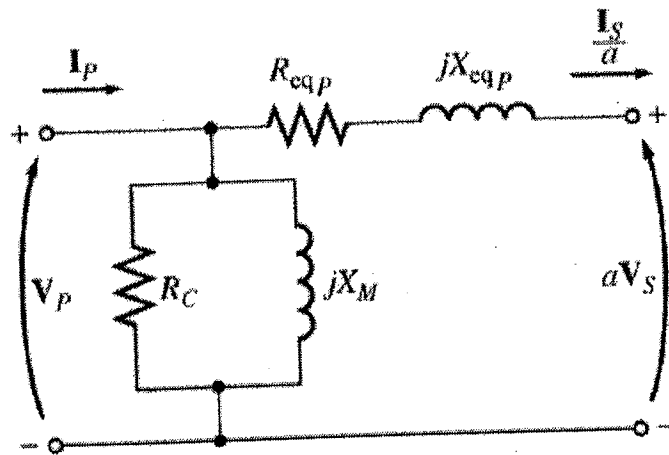


Figure 1: Approximate equivalent circuit of the transformer referred to the primary side

Determine the followings,

- i. the primary current of the transformer.
- ii. voltage regulation of the transformer.
- iii. input power of the transformer.
- iv. output power of the transformer.
- v. efficiency of the transformer.

(25 marks)

- b. A single phase auto transformer has a voltage ratio of 320 V: 250 V and supplies a load of 20 kVA at 250 V. Assuming an ideal transformer, determine the followings,

- i. draw an appropriate model for the above auto transformer
- ii. calculate the current in each section of the winding

(10 marks)

3.

a. Explain how induction torque is generated in an induction motor.

(03 marks)

b. A three-phase, 60 Hz induction motor runs at 890 rad/min at no load and at 840 rad/min at full load. Determine the followings,

- i. number of poles in this motor.
- ii. the slip at rated load.
- iii. the speed at one-quarter (1/4) of the rated load.
- iv. the electrical frequency of the rotor at one-quarter (1/4) of the rated load.

(12 marks)

c. A 208 V, 60 Hz Y connected wound rotor induction motor is rated at 15 hp. Its circuit components are

$$R_1 = 0.200 \Omega \quad R_2 = 0.120 \Omega \quad X_M = 15.0 \Omega$$

$$X_1 = 0.410 \Omega \quad X_2 = 0.410 \Omega$$

$$P_{\text{mech}} = 250 \text{ W} \quad P_{\text{misc}} = 0 \quad P_{\text{core}} = 180 \text{ W}$$

For a slip of 0.05 calculate the followings,

- i. the line current, I_L .
- ii. the stator copper losses, P_{SCL} .
- iii. the air gap power P_{AG} .
- iv. the power converted from electrical to mechanical form, P_{CONV} .
- v. the induced torque, T_{ind} .
- vi. the load torque, T_{load} .
- vii. the overall machine efficiency.
- viii. the motor speed in rev/min and rad/sec.

(20 marks)

