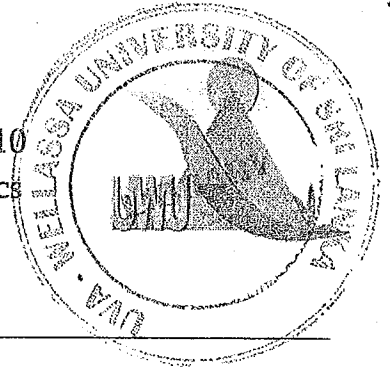


Uva Wellassa University, Sri Lanka
End Semester Examination – August 2010
SCT 161-1 Basic Electricity & Electronics



Time: One (01) hour

Total 03 Questions

Answer All questions.

- 1) a. What is the Superposition theorem?
- b. A storage battery X has an e.m.f. of 6V and an internal resistance of 2Ω . Another battery Y has an e.m.f. of 4V and an internal resistance of 2Ω . The two batteries are connected in parallel across a resistance of 10Ω as in Fig Q1. By using the Superposition theorem determine the current in each branch of the network.

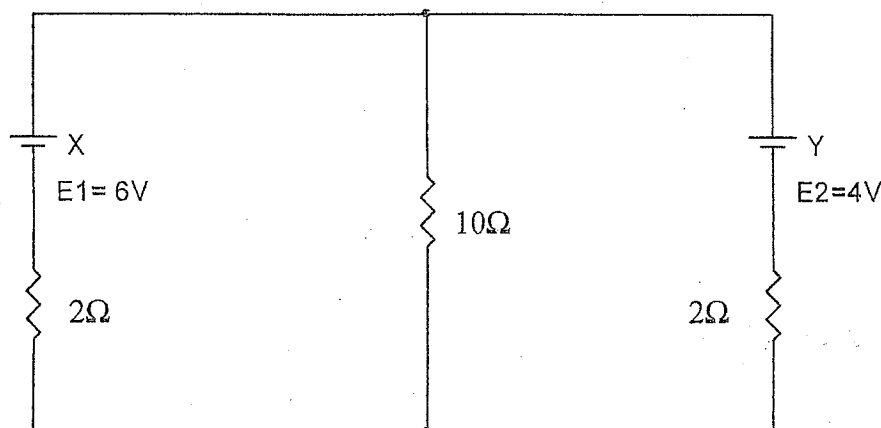


Fig Q1

(30 Marks)

- 2) a. What is the armature of a DC generator? What are the main types of windings of an armature?
- b. Write down the EMF equation of a DC generator. Explain the terms of your equation.
- c. A short shunt cumulative compound DC generator supplies 8kW at 200V. The shunt field, series field and armature resistance are 100, 0.2 and 0.4Ω respectively. Calculate
- i. Induced e.m.f.
 - ii. Load resistance

(40 Marks)

- 3) a. What is the back e.m.f. of a DC motor? Derive the relation for the back e.m.f. and the supplied voltage in terms of armature resistance.
- b. A 230V DC motor has an armature system of 0.6Ω . If the full load armature current is 30A and the no load armature current is 4A. Calculate the back e.m.f. at
- i. no load
 - ii. full load

(30 Marks)