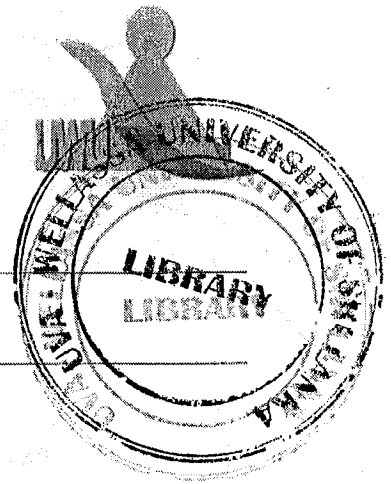


Uva Wellassa University, Sri Lanka  
End Semester Examination – January 2010  
SCT 253-1 Applied Electricity

Time: One (01) hour

Total 04 Questions  
Answer All questions.



- 1) a. Explain the terms reactance and impedance.  
b. What is meant by "True power" and "Apparent power" of *RLC* circuit?  
c. A coil of resistance  $40\Omega$  and inductance  $25\text{ mH}$  in series with a  $25\ \mu\text{F}$  capacitor is connected to a sinusoidal voltage source of  $250\text{ V}$  and frequency of  $100\text{ Hz}$  as shown in Fig Q1.

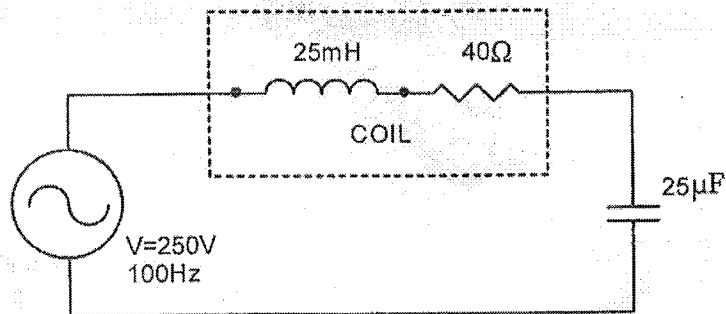


Fig Q1

Calculate

- i. reactance of the coil
- ii. reactance of the capacitor
- iii. impedance of the circuit
- iv. current
- v. voltage across the coil
- vi. voltage across the capacitor
- vii. True power and power factor
- viii. Draw the phasor diagram

(40 Marks)

- 2) a. What is a series resonant circuit?  
b. Obtain an expression for resonant frequency ( $f_0$ ) of series *L-C* circuit.  
c. A circuit must be designed to have  $f_0 = 9.00\text{ MHz}$ . You have given a  $33\text{ pF}$  fixed capacitor. What is the inductance of coil (*L*) will be needed to get the desired resonant frequency?

(20 Marks)

3) A coil is wound uniformly with 400 turns over a steel ring of relative permeability 900 having a mean circumference length of 50 cm and a cross sectional area of 5 cm<sup>2</sup> (Fig Q3). If the coil has a resistance of 125Ω and is connected to 250 V DC supply, calculate

- a. Current through the coil
- b. The coil m.m.f.
- c. The coil magnetic field strength
- d. Total magnetic flux
- e. Reluctance of the ring
- f. Permeance of the ring

Where permeability of free space is  $4\pi \times 10^{-7}$  H/m

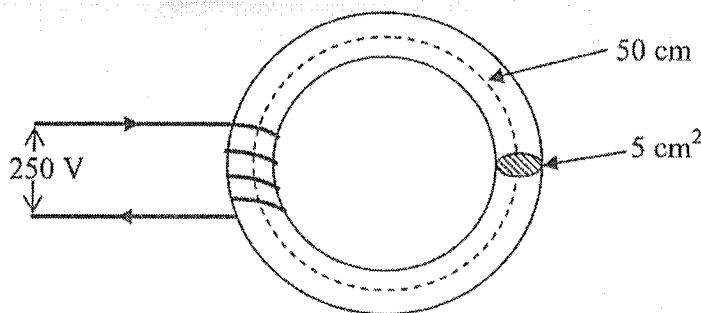


Fig Q3

(25 Marks)

- 4) a. What are the main types of Transformer losses?
- b. The step-down transformer at a power factor of unity is designed to deliver 240 V to a load of 5 kW. The transformer's primary winding is connected to a 600 V source, Find the current in
- i. the load
  - ii. the primary winding.

(15 Marks)