

Instructions to candidates

Duration: 02 hours

Number of questions: 03 Essay

Mark allocation: 200 marks


Answer all questions.

1.

a. State Ohm's law and Kirchoff's laws.


(15 marks)

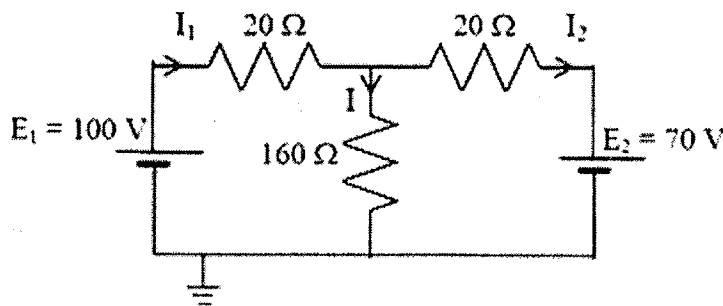b. Find the current (I) through 160Ω resistor.



(20 marks)

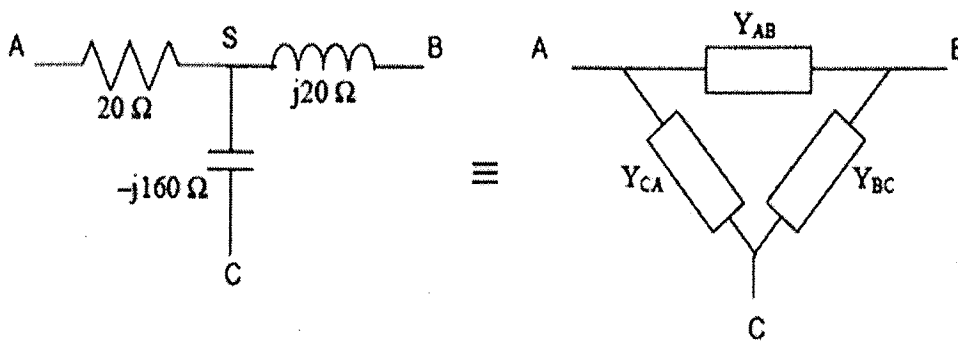c. Determine the **Delta** equivalent of the **Star** connected network shown below.



(20 marks)


d. Briefly explain

- i. Reciprocity theorem
- ii. Norton's theorem
- iii. Passive network
- iv. Active network

(20 marks)


2.

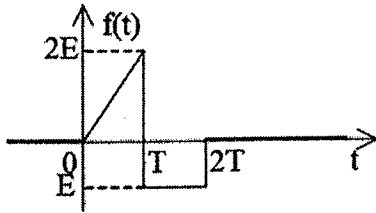a. Find the Laplace transformation of the following waveforms.




(25 marks)

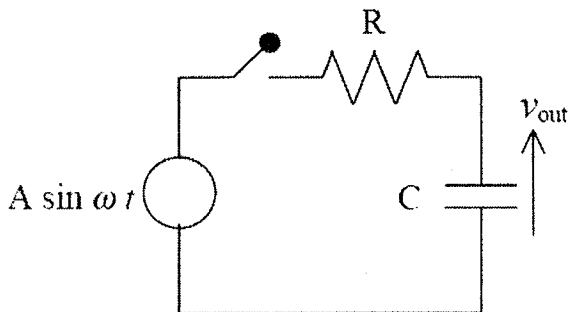b. Determine the transient voltage V_{out} across the capacitor C when the switch is closed at time $t=0$. Capacitor C is initially uncharged.



(25 marks)

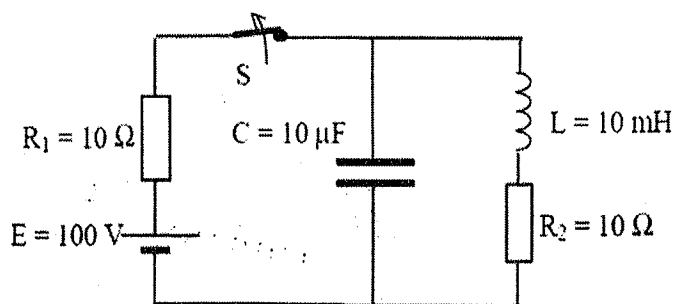c. Figure shows a circuit which has reached steady state with switch S closed. If the switch S is opened at time $t=0$, obtain an expression for the ensuing current through the inductor, L .



(25 marks)


3.

a. A three phase 400V, 50Hz, balanced supply feeds a balanced load consisting of three equal single phase loads of $(40 + j30)\Omega$ connected in Star.

Determine,

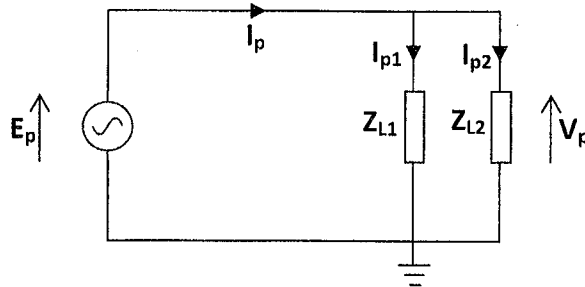- (i) the supply current,
- (ii) supply power factor,
- (iii) active and reactive power supplied
- (iv) and the value of the capacitance that must be connected in Delta to improve the overall power factor to 0.95 lag.



Note: Obtain the result using any one phase in the three phase system.



(35 marks)

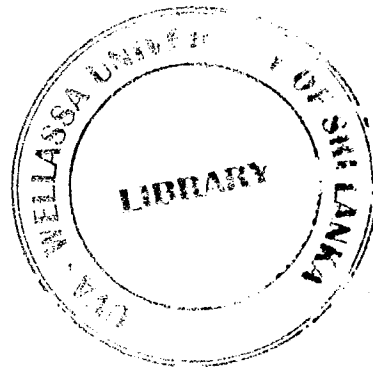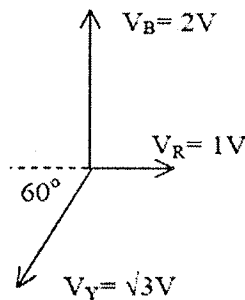a. Find the symmetrical components of the unbalanced system of the following voltages.

$$1 \angle 0^\circ \text{V}, \sqrt{3} \angle -120^\circ \text{V} \text{ and } 2 \angle 90^\circ \text{V}.$$



(15 marks)