

Instructions to candidates

Duration: 01 hour

Number of questions: 02

Answer all questions

Mark allocation: 100

1.

- a. Write a relationship among turns ratio, voltage ratio, and current ratio of an ideal transformer.

(12 marks)

- b. Calculate the voltage and current through the load resistor R_L in the circuit given in Figure 01 below.

(12 marks)

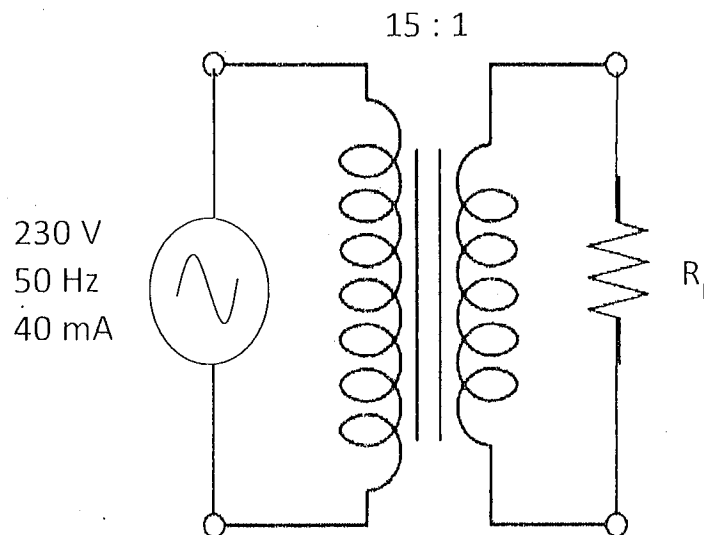


Figure 01

- c. Draw the wave form through the load resistor R_L in Figure 01.

(06 marks)



- d. An ideal transformer, connected to a 240 V main power supply, has a secondary circuit which consists of a 16 V, 120 W lamp. Calculate the transformer turns ratio and the current taken from the primary circuit.

(20 marks)

2.

- a. An *npn* transistor is biased in the forward-active mode. The base current (I_B) is $8.50 \mu\text{A}$ and the current gain beta (β) is 150. Determine I_C , I_E and alpha (α).

(20 marks)

- b. Calculate I_B , I_C , I_E , and V_{CE} for the following circuit, given that $\beta = 100$ and $V_{BE} = 0.7 \text{ V}$.

(30 marks)

