

CST 101-3 Basic Electricity and Electronics (Repeat)

**Instructions to candidates**

Duration: 03 Hours.

Number of questions: 06

Answer **all** questions.

Mark allocation: 180

1.

a) State Kirchoff's current law and Kirchoff's voltage law.

(10 marks)

b) Calculate the current through the resistors  $R_1$ ,  $R_2$ , and  $R_3$  in the circuit diagram shown in Figure 01 below using Kirchoff's laws.

Clearly illustrate the steps.

(25 marks)

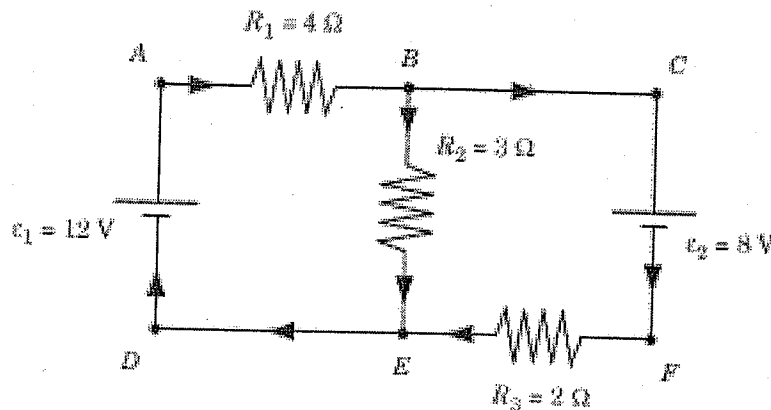


Figure 01



2.  
a. State the thevenin's theorem.

(10 marks)

- b. Calculate the current through the  $1.25\text{ k}\Omega$  resistor in the following circuit in Figure 02 using Thevenin's theorem. Clearly illustrate the steps. Also calculate the power dissipated in the  $1.25\text{ k}\Omega$  resistor.

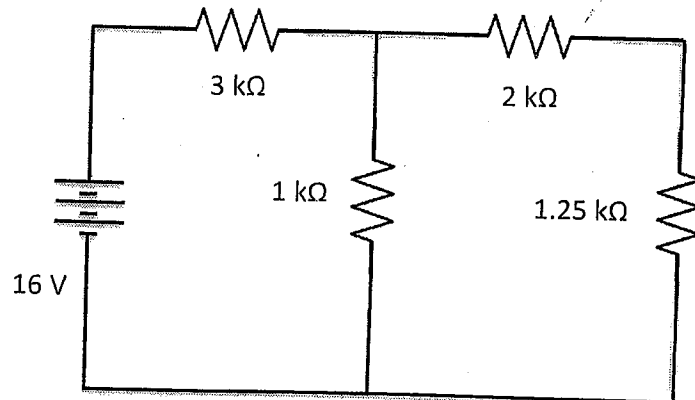


Figure 02


(30 marks)

3.  
a. Write a relationship between turns ratio, voltage ratio, and current ratio of an ideal transformer.

(06 marks)

- b. Assuming the circuit diagram shown in Figure 03 is an ideal transformer, calculate current and voltage in the secondary coil.

(06 marks)

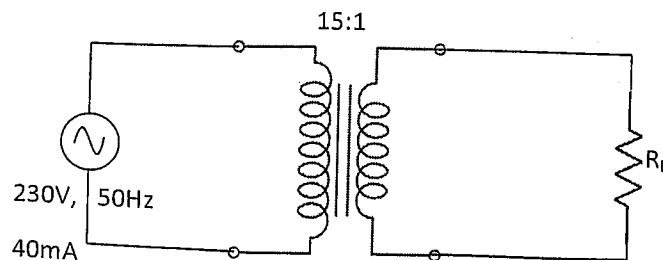

c. Draw the detailed output waveform through  $R_L$  of the above circuit.

(03 marks)

4.

a. An *npn* transistor is biased in the forward-active mode. The base current ( $I_B$ ) is  $7.50 \mu\text{A}$  and the collector current ( $I_C$ ) is  $1.50 \text{ mA}$ . Determine current gain ( $\beta$ ) and emitter current ( $I_E$ ).

(12 marks)

b. Calculate  $I_B$ ,  $I_C$ ,  $I_E$  and  $V_{CE}$  for the following circuit shown in Figure 04, given that  $\beta = 100$  and  $V_{BE} = 0.7 \text{ V}$ .

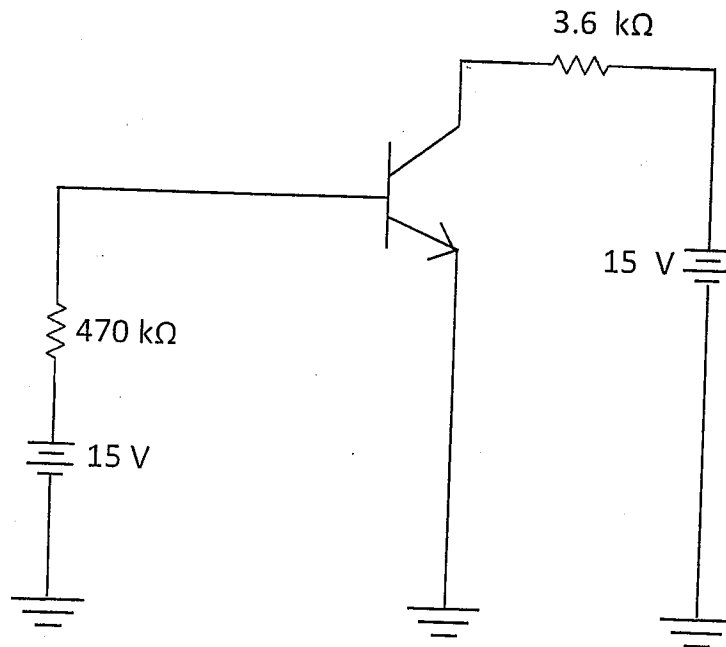


Figure 04

(18 marks)



5.

a. Draw a detailed circuit diagram of a center tapped full wave rectifier.

(07 marks)

b. For a center tapped transformer the primary rms voltage value is 230 V. The primary winding to secondary winding turn ratio is 20 : 1. Note that  $V_{rms} = 0.707 V_{peak}$

I. What is the peak primary voltage ?

(04 marks)

II. What is the peak secondary voltage ?

(04 marks)

c. A center tapped full wave rectifier is connected to the transformer.

I. What is the peak input voltage ?

(05 marks)

II. What is the peak output voltage ?

(05 marks)

III. Draw the input and output wave forms for the rectifier.

(10 marks)

6.

a. What is the main function of a DC motor ?

(04 marks)

b. Write down the four major parts of a DC motor.

(04 marks)

c. Write short notes about the above mentioned four parts.

(12 marks)

d. What is the unique characteristic of a zener diode ?

(05 marks)