

Uva Wellassa University of Sri Lanka
Faculty of Science and Technology
Department of Computer Science and Technology
100 level 2nd Semester Examination – Dec./Jan. 2016/17
CST161-3 Microcomputer Architecture and Logic Design



Instructions to candidates

Duration: Two (02) hours

Number of questions: Four (04)

Answer all questions

Mark allocation: 100

1.
 - a. Define positive logic system and negative logic system? (4 mark)
 - b. Simplify the Boolean expression $xy + x(wz + wz')$ to a minimum number of literals. (2 mark)
 - c. Draw logic diagrams for the original and simplified expressions in **part b**. (4 mark)
 - d. Express the Boolean function $F = xy + x'z$ as a product of sums. (4 mark)
 - e. Convert the function $F(A,B,C) = \sum(1,4,5,6,7)$ into the form of **Maxterms** by taking the complement of the original function. (5 mark)
 - f. Simplify the Boolean function $F(A,B,C,D) = \sum(0,2,4,5,6,7,8,10,13,15)$ using a Karnaugh map. (6 mark)

2.
 - a. Explain why the carry propagation time is an important attribute of the adder. (5 mark)
 - b. Implement a full adder with two (02) **4x1 multiplexers**. (5 mark)
 - c. Implement a full adder with a **3x8 decoder**. (5 mark)
 - d. Design a combinational circuit that converts the **8,4,-2,-1 code to Gray code**. A truth table, Boolean equations and a logic diagram should be included. (10 mark)



3.

- a. What is a sequential circuit? (2 mark)
- b. Draw a block diagram of a D flip-flop constructed using D latches with an enable pin and explain the operation of it. (4 mark)
- c. Analyze the circuit given in Figure 1 and draw the state diagram (Hint: JK flip-flop characteristic table is given in Table 1). (7 mark)

Table 1: JK Flip-Flop Characteristic Table

JK Flip-Flop			
J	K	Q(t+1)	Note
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

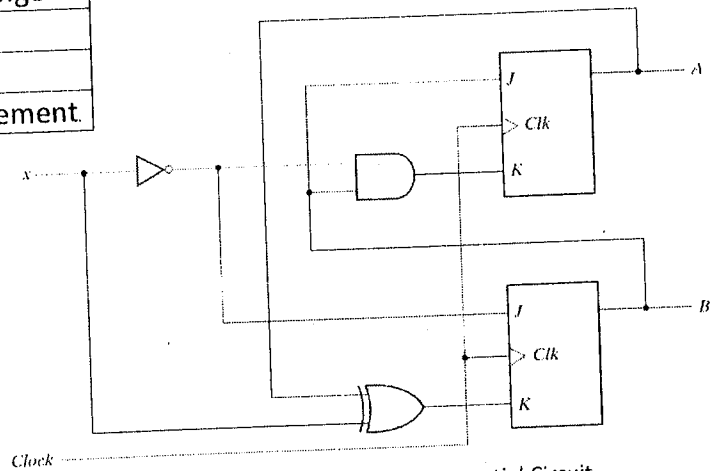


Figure 1: Sequential Circuit

- d. Design a three-bit binary counter using T flip-flops by following the steps given below.

- i. Draw the state diagram
- ii. Draw the state table
- iii. Derive T flip-flop input equations
- iv. Draw the logic diagram

(12 mark)

4.

- a. Explain the difference between **Mealy** model and **Moore** model. (4 mark)
- b. Differentiate a register and a counter. (4 mark)
- c. Explain the main difference of ripple counter and synchronous counter. (4 mark)
- d. Draw the logic diagram of a **four-bit** shift register using **D flip-flops**. (4 mark)
- e. Design a **four-bit** serial adder using shift registers and other required components. (9 mark)